PEARSON EDEXCEL A-LEVEL PHYSICS · 9PH0

PHYSICS



EXAM QUESTION PACK

TOPIC 7: ELECTRIC AND MAGNETIC FIELDS

CAPACITANCE

SCORE	PERCENTAGE
/288	%

STEMUP

These questions belong to Pearson Edexcel, not to us.

The examination questions and mark schemes in this pack were written and published by Pearson Edexcel. They are past assessment materials, reproduced here so that students can revise from them.

What we do not own

STEMUP is not affiliated with Pearson Edexcel and does not own, and makes no claim to own, any of the question or mark scheme material in this pack. Pearson has not endorsed, approved or been involved in the production of it. Pearson, Edexcel and the qualification titles used here belong to their respective owners and appear for identification only.

Where to find the originals

Pearson publishes its past papers and mark schemes free of charge. Always check the current specification at qualifications.pearson.com before you revise, because content and wording can change between series.

If you hold the rights to any material in this pack and would like it amended or removed, contact admin@stemup.co.uk and we will act on it.

Q1.

A defibrillator is an electrical device designed to deliver a brief electrical signal to restore a normal rhythm to the heart. Electrodes are attached to the chest of a patient and a charged capacitor is discharged through the chest cavity.

In one defibrillator a 56 μF capacitor is charged by a potential difference of 2500 V.
During the discharge of the capacitor the resistance between the electrodes is 45 Ω.

Show that the time taken for 99% of the discharge to take place is about 12 ms and hence calculate the average current delivered by the defibrillator during this period.

(6)

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

Average current = ...

(Total for question = 6 marks)

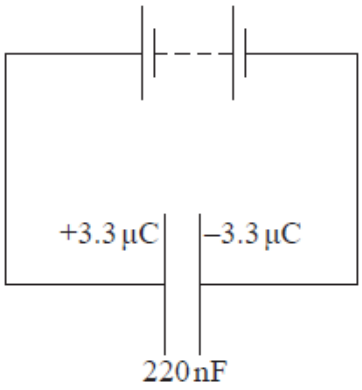Q2.

A capacitor is charged by a battery as shown in the circuit diagram.



(a) Calculate the e.m.f. of the battery and the energy stored in the charged capacitor.

(4)

.....

.....

.....

.....

.....

E.m.f. = ...

Energy = ...

(b) The capacitor is disconnected from the battery and discharged through a 20 MΩ resistor.

Calculate the time taken for 80% of the charge on the capacitor to discharge through the resistor.

(3)

.....

.....

.....

.....

.....

.....

.....

Time taken = ...

(c) Use an equation to explain whether the time taken for the capacitor to lose half its energy is greater or less than the time taken to lose half its charge.

(3)

.....

.....

.....

.....

.....

.....

(d) A student carries out an experiment to record data so that she can plot a graph of potential difference against time as the capacitor discharges.

State **two** advantages of using a datalogger rather than a voltmeter and stopwatch to record this data.

(2)

.....

.....

.....

.....

(Total for question = 12 marks)

Q3. A student is investigating how the potential difference across a capacitor varies with time as the capacitor is charging.

He uses a 100 μF capacitor, a 5.0 V d.c. supply, a resistor, a voltmeter and a switch.

(a) (i) Draw a diagram of the circuit he should use.

(2)

(ii) Suggest why a voltage sensor connected to a data logger might be a suitable instrument for measuring the potential difference across the capacitor in this investigation.

(1)

.....

.....

(b) Calculate the maximum charge stored on the capacitor.

(2)

.....


.....

.....

.....

Charge = ...

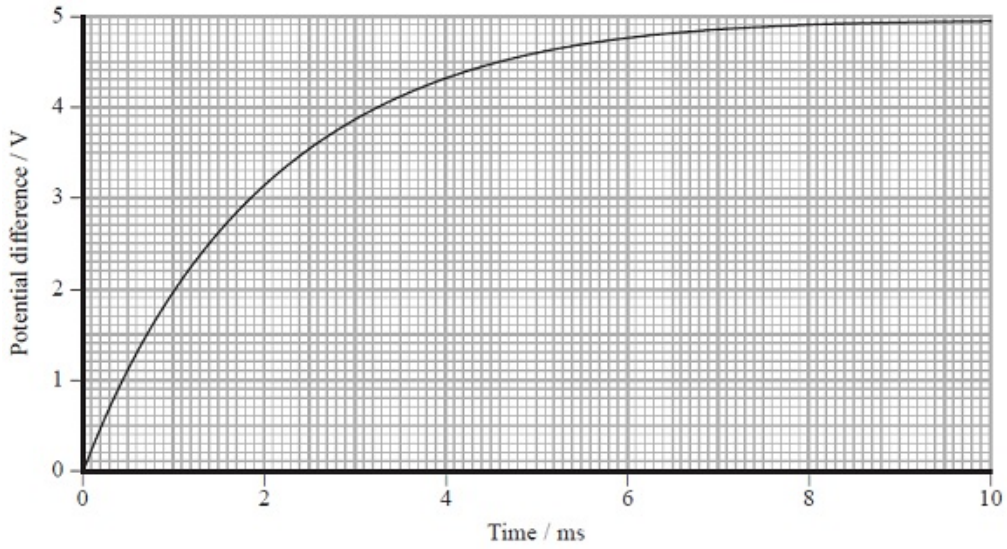(c) The graph shows how the potential difference across the capacitor varies with time as the capacitor is charging.



(i) Estimate the average charging current over the first 10 ms.

(2)

.....

.....

.....

Average charging current = ...

(ii) Use the graph to estimate the initial rate of increase of potential difference across the capacitor and hence find the initial charging current.

(3)

.....

.....

.....

.....

.....

.....

.....

Initial charging current = ...

(iii) Use the value of the initial charging current to find the resistance of the resistor.

(2)

.....

.....

.....

.....

Resistance = ...

(Total for Question = 12 marks)

Q4. A particular experiment requires a very large current to be provided for a short time.

(a) An average current of 2.0×10^3 A is to be supplied to a coil of wire for a time of 1.4×10^{-3} s. The resistance of the coil is 0.50 Ω.

(i) Show that the charge that flows through the coil during this time is about 3 C.


(2)

.....

.....

.....

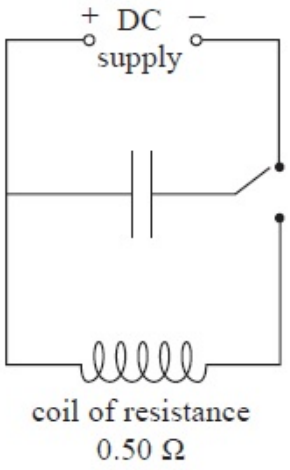(ii) The circuit shows how a capacitor could be charged and then discharged through the coil to provide the current.



The circuit contains a capacitor of capacitance 600 μF. This capacitor is suitable to provide the current for 1.4×10^{-3} s.

Explain why the capacitor is suitable.

(3)

.....

.....

.....

.....

.....

.....

(b) It can be assumed that the 600 μF capacitor completely discharges in 1.4×10^{-3} s.

(i) Calculate the potential difference of the power supply.

(2)

.....

.....

.....

Potential difference = ...

(ii) Calculate the average power delivered to the coil in this time.

(3)

.....

.....

.....

.....

.....

.....

Average power = ...

(Total for Question = 10 marks)

Q5.

In recent years there has been a development of ultracapacitors which have much higher capacitance than traditional capacitors. Capacitors store energy due to charge in an electric field whereas batteries store energy due to a chemical reaction. There are several applications where ultracapacitors have an advantage over batteries; for example storing energy from rapidly fluctuating supplies or delivering charge very quickly.

(a) A typical ultracapacitor has a capacitance of 1500 F and a maximum operating potential difference of 2.6 V.

(i) Show that the charge on this capacitor when fully charged is about 4000 C.

(2)


.....

.....

.....

(ii) Complete the graph on the axes below to show how the potential difference varies with charge for this capacitor.

(2)

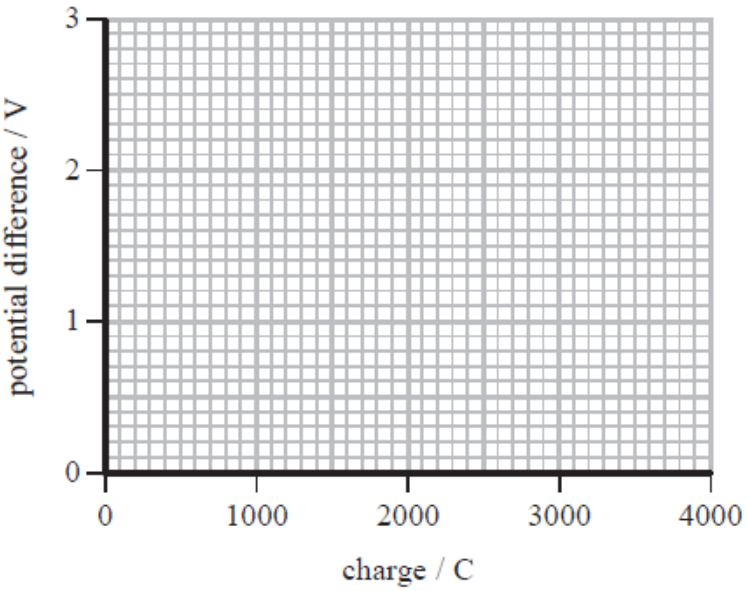

(iii) Calculate the energy stored in this capacitor when fully charged.

(2)


.....

.....

.....

Energy = ...

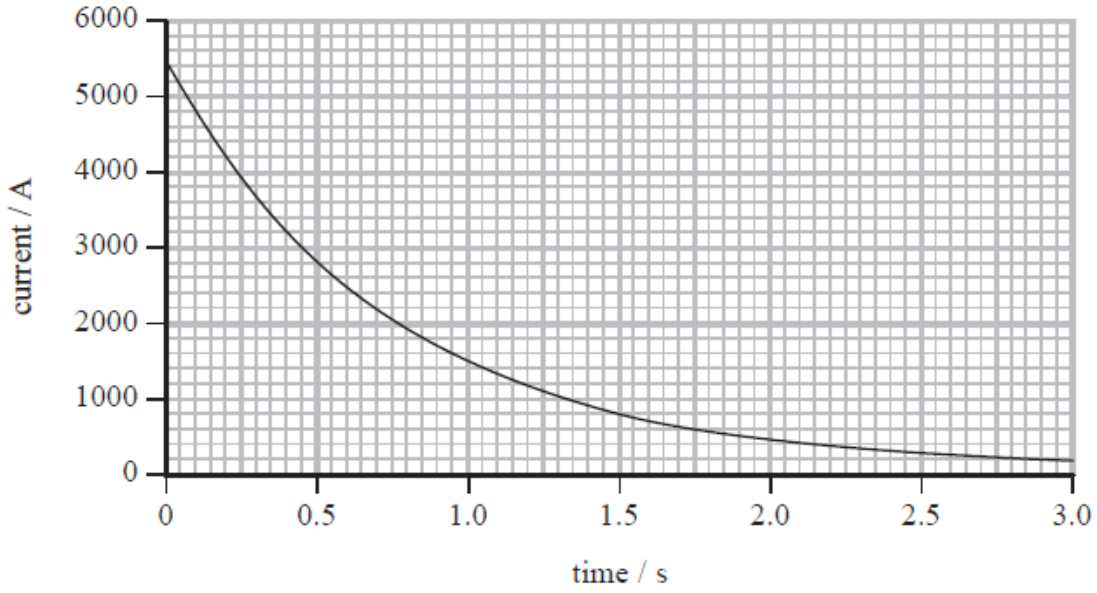(b) The graph below shows how the current varies with time as the capacitor is discharged through a circuit.



(i) Describe and explain the shape of the graph.

(2)

.....

.....

.....

.....

.....

(ii) Calculate the resistance of the circuit.

(4)

.....

.....

.....

.....

.....

Resistance = ...

(c) There is a limit to the amount of charge an ultracapacitor can hold but it can deliver the charge very quickly. A battery can deliver much more charge but only at a slower rate. For electric powered vehicles it is suggested that using a combination of batteries and ultracapacitors would give the best performance.

Suggest, with reasons, which stages of a journey would be more suited to ultracapacitors and which would be more suited to batteries.

(3)

.....

.....

.....

.....


.....

.....

(Total for question = 15 marks)

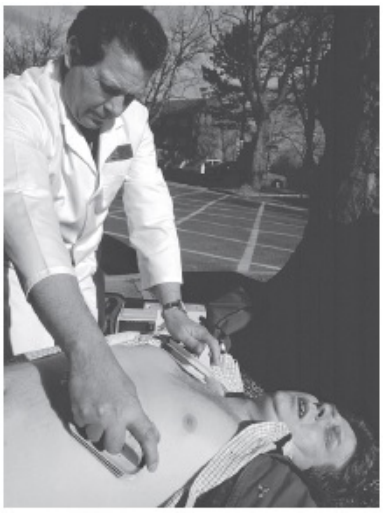
Q6.

A defibrillator is a machine that is used to correct an irregular heartbeat or to start the heart of someone who is in cardiac arrest.



The defibrillator passes a large current through the heart for a short time.

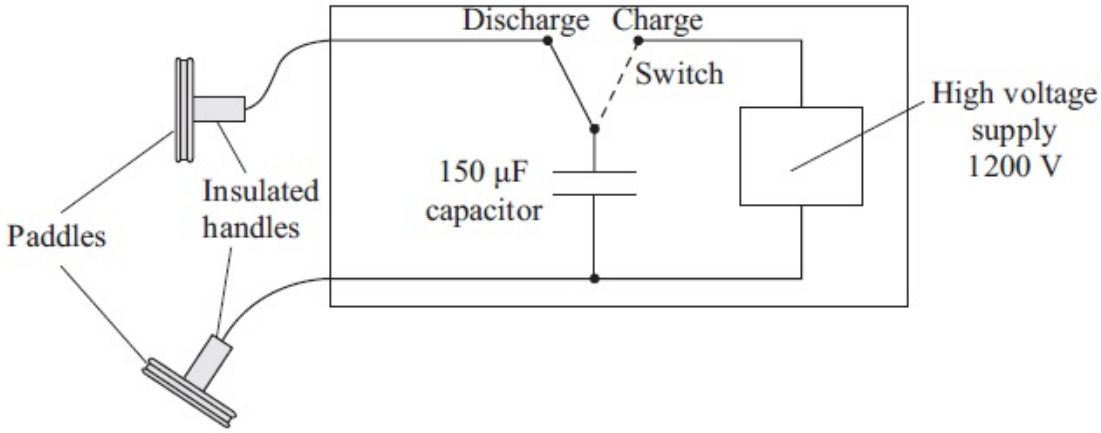The machine includes a high voltage supply which is used to charge a capacitor. Two defibrillation 'paddles' are placed on the chest of the patient and the capacitor is discharged through the patient.



(a) The 150 μF capacitor is first connected across the 1200 V supply

Calculate the charge on the capacitor.

(2)

.....

.....

Charge = ...

(b) Calculate the energy stored in the capacitor.

(2)

.....

.....

.....

Energy stored = ...

(c) When the capacitor discharges there is an initial current of 14 A in the chest of the patient.

(i) Show that the electrical resistance of the body tissue between the paddles is about 90 Ω

(1)

.....

.....

(ii) Calculate the time it will take for three quarters of the charge on the capacitor to discharge through the patient.

(3)

.....

.....

.....

.....

.....

Time = ...

(iii) Body resistance varies from person to person. If the body resistance was lower, the initial current would be greater.

State how this lower body resistance affects the charge passed through the body from the defibrillator.

(1)

.....

.....


.....

(Total for question = 9 marks)

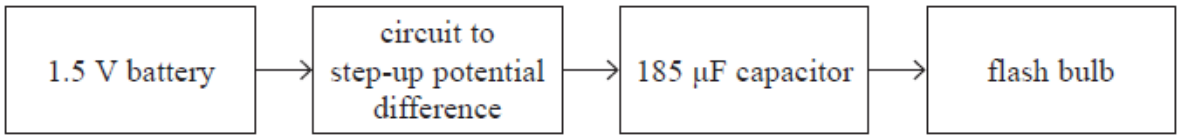Q7.

* Cameras usually have an inbuilt flash bulb that can be used to take photographs in poor light conditions. As a photograph is taken, the bulb should be able to produce a bright flash of light for up to 4 ms.

A capacitor can be used along with a battery as a power supply for the flash bulb. The flow diagram shows a possible arrangement.



Comment on the suitability of using this capacitor arrangement as a power supply rather than connecting the bulb directly to the battery.

A typical flash bulb has a resistance of 6 Ω.

(6)

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

(Total for question = 6 marks)

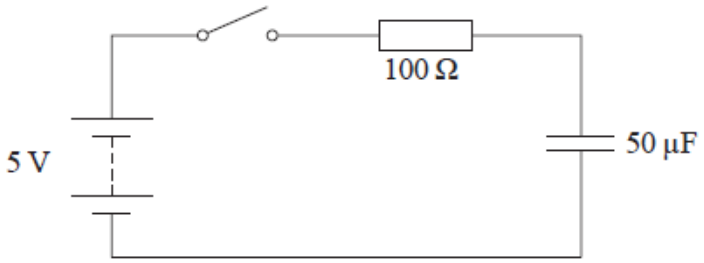Q8.

A circuit consists of a battery of e.m.f. 5 V and negligible internal resistance, a switch, a 100 Ω resistor and an uncharged 50 μF capacitor.



Describe what happens to the potential difference across the resistor and the potential difference across the capacitor after the switch is closed.

(4)

.....

.....

.....

.....

.....

.....

.....

.....

(Total for question = 4 marks)

Q9.

A capacitor of capacitance C is charged to a potential difference V by a power supply.
The energy stored on the charged capacitor is W.

What would be the energy stored if the potential difference were $2V$?

(1)

☒ **A** $\frac{W}{4}$

☒ **B** $\frac{W}{2}$


☒ **C** $2W$

☒ **D** $4W$

(Total for question = 1 mark)

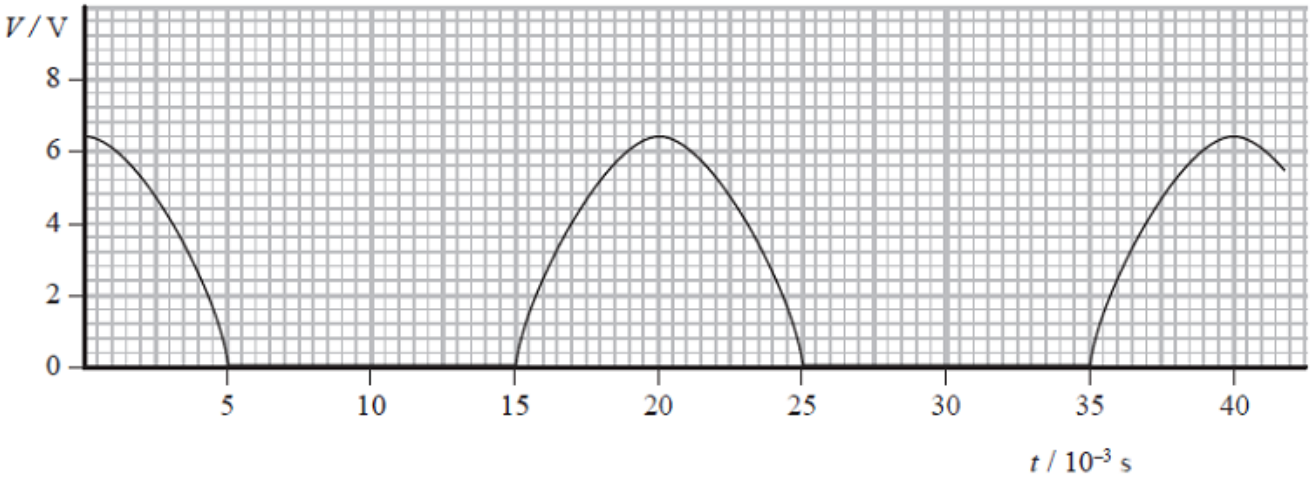Q10.

The graph shows how the output V from the terminals of a power supply labelled d.c. (direct current) varies with time t. This type of supply will not allow current to flow backwards through it.



(a) A student connects a capacitor across the terminals of this power supply in order to try to produce a constant voltage.

Suggest how this produces a constant voltage.

(2)


.....

.....


.....

.....

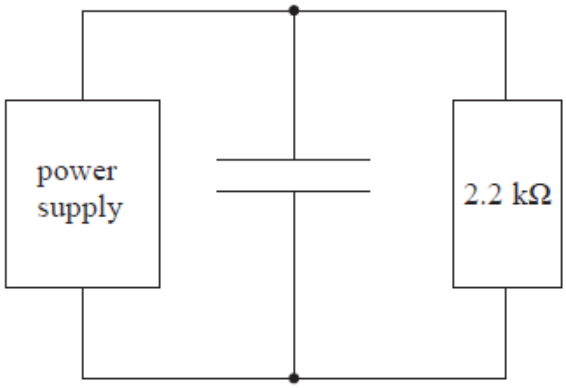(b) The student then connects a resistor across the capacitor as shown.



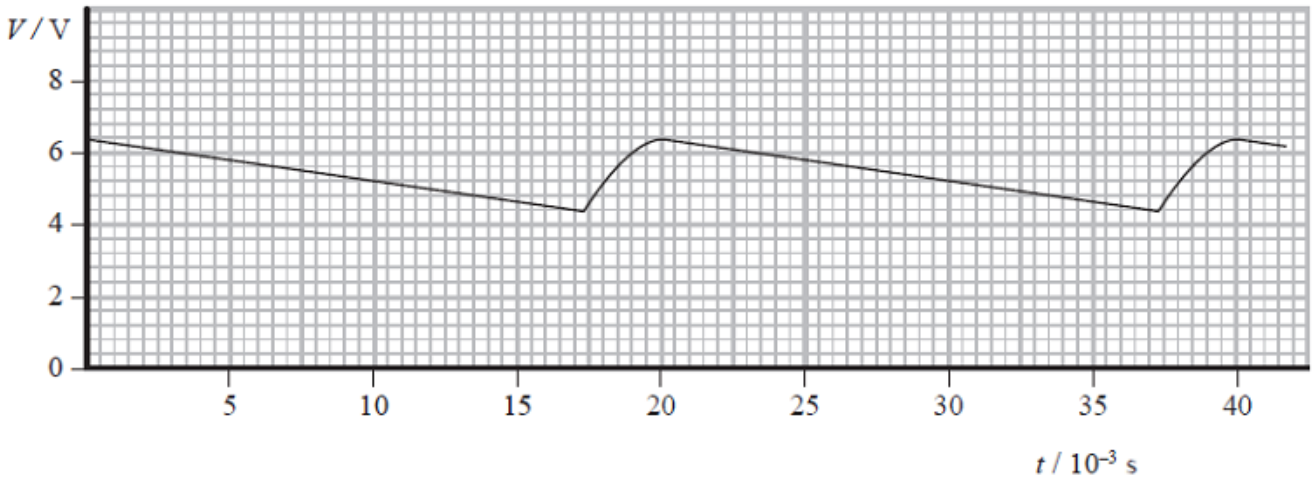The graph shows the variation of the potential difference V across the resistor with time t.



(i) Estimate the average potential difference across the resistor.

(1)

.....

.....

Average potential difference = ...

(ii) Calculate the average current in the resistor.

(2)

.....

.....

Average current = ...

(iii) Determine the time in each cycle for which the capacitor discharges through the resistor.

(1)

.....

.....

Discharge time = ...

(iv) Calculate the charge passing through the resistor during one discharge of the capacitor and hence determine the capacitance of the capacitor.

(4)

.....

.....

.....

.....

.....

.....

.....

.....

Charge = ...

Capacitance = ...

(c) The student wants to produce a potential difference across the same resistor that has less variation in magnitude.
State, with a reason, what the student could do to achieve this.

(2)

.....

.....


.....

.....

(Total for question = 12 marks)

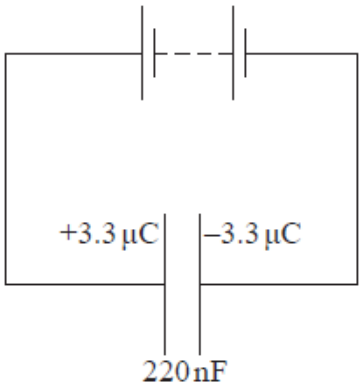Q1.

A capacitor is charged by a battery as shown in the circuit diagram.



(a) Calculate the e.m.f. of the battery and the energy stored in the charged capacitor.

(4)

.....

.....

.....

.....

.....

E.m.f. = ...

Energy = ...

(b) The capacitor is disconnected from the battery and discharged through a 20 MΩ resistor.

Calculate the time taken for 80% of the charge on the capacitor to discharge through the resistor.

(3)

.....

.....

.....

.....

.....

.....

.....

Time taken = ...

(c) Use an equation to explain whether the time taken for the capacitor to lose half its energy is greater or less than the time taken to lose half its charge.

(3)

.....

.....

.....

.....

.....

.....

(d) A student carries out an experiment to record data so that she can plot a graph of potential difference against time as the capacitor discharges.

State **two** advantages of using a datalogger rather than a voltmeter and stopwatch to record this data.

(2)

.....

.....

.....

.....

(Total for question = 12 marks)

Q2. A particular experiment requires a very large current to be provided for a short time.

(a) An average current of 2.0×10^3 A is to be supplied to a coil of wire for a time of 1.4×10^{-3} s. The resistance of the coil is 0.50 Ω.

(i) Show that the charge that flows through the coil during this time is about 3 C.


(2)

.....

.....

.....

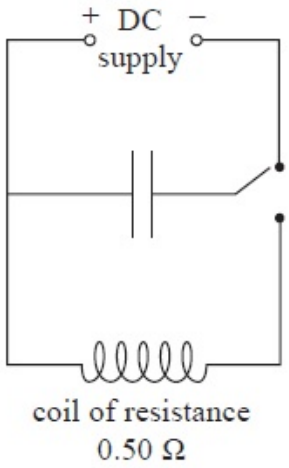(ii) The circuit shows how a capacitor could be charged and then discharged through the coil to provide the current.



The circuit contains a capacitor of capacitance 600 μF. This capacitor is suitable to provide the current for 1.4×10^{-3} s.

Explain why the capacitor is suitable.

(3)

.....

.....

.....

.....

.....

.....

(b) It can be assumed that the 600 μF capacitor completely discharges in 1.4×10^{-3} s.

(i) Calculate the potential difference of the power supply.

(2)

.....

.....

.....

Potential difference = ...

(ii) Calculate the average power delivered to the coil in this time.

(3)

.....

.....

.....

.....

.....

.....

Average power = ...

(Total for Question = 10 marks)

Q3.

In recent years there has been a development of ultracapacitors which have much higher capacitance than traditional capacitors. Capacitors store energy due to charge in an electric field whereas batteries store energy due to a chemical reaction. There are several applications where ultracapacitors have an advantage over batteries; for example storing energy from rapidly fluctuating supplies or delivering charge very quickly.

(a) A typical ultracapacitor has a capacitance of 1500 F and a maximum operating potential difference of 2.6 V.

(i) Show that the charge on this capacitor when fully charged is about 4000 C.

(2)


.....

.....

.....

(ii) Complete the graph on the axes below to show how the potential difference varies with charge for this capacitor.

(2)

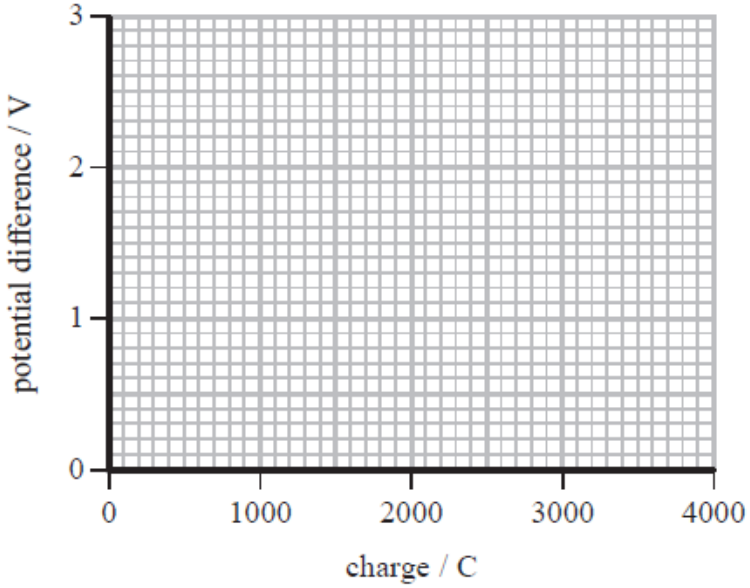

(iii) Calculate the energy stored in this capacitor when fully charged.

(2)


.....

.....

.....

Energy = ...

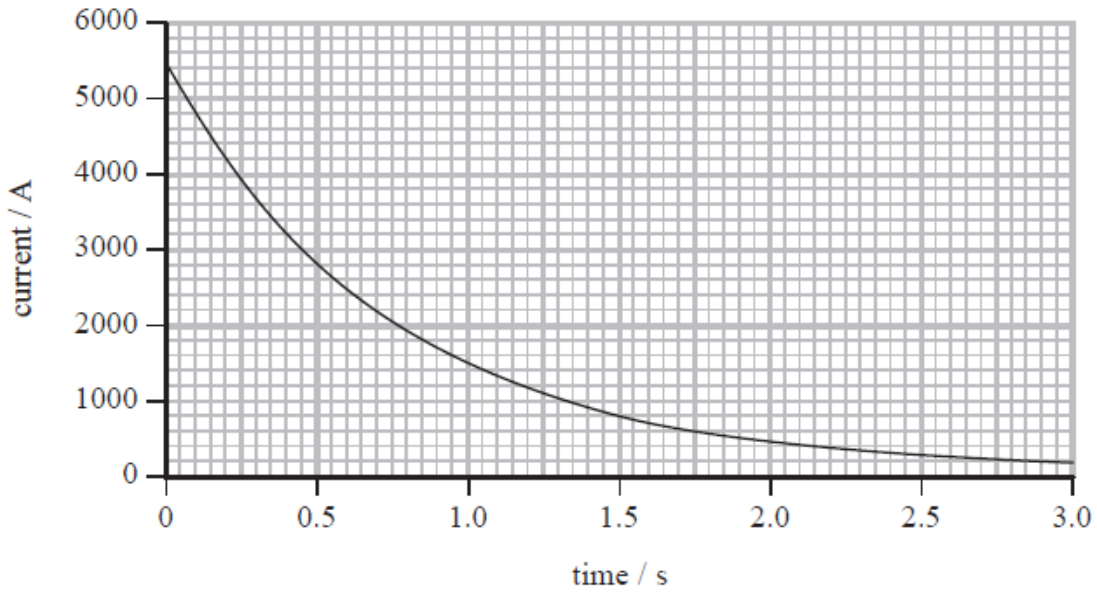(b) The graph below shows how the current varies with time as the capacitor is discharged through a circuit.



(i) Describe and explain the shape of the graph.

(2)

.....

.....

.....

.....

.....

(ii) Calculate the resistance of the circuit.

(4)

.....

.....

.....

.....

.....

Resistance = ...

(c) There is a limit to the amount of charge an ultracapacitor can hold but it can deliver the charge very quickly. A battery can deliver much more charge but only at a slower rate. For electric powered vehicles it is suggested that using a combination of batteries and ultracapacitors would give the best performance.

Suggest, with reasons, which stages of a journey would be more suited to ultracapacitors and which would be more suited to batteries.

(3)

.....

.....

.....

.....


.....

.....

(Total for question = 15 marks)

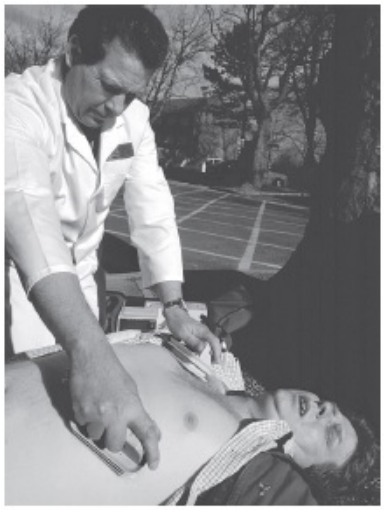
Q4.

A defibrillator is a machine that is used to correct an irregular heartbeat or to start the heart of someone who is in cardiac arrest.



The defibrillator passes a large current through the heart for a short time.

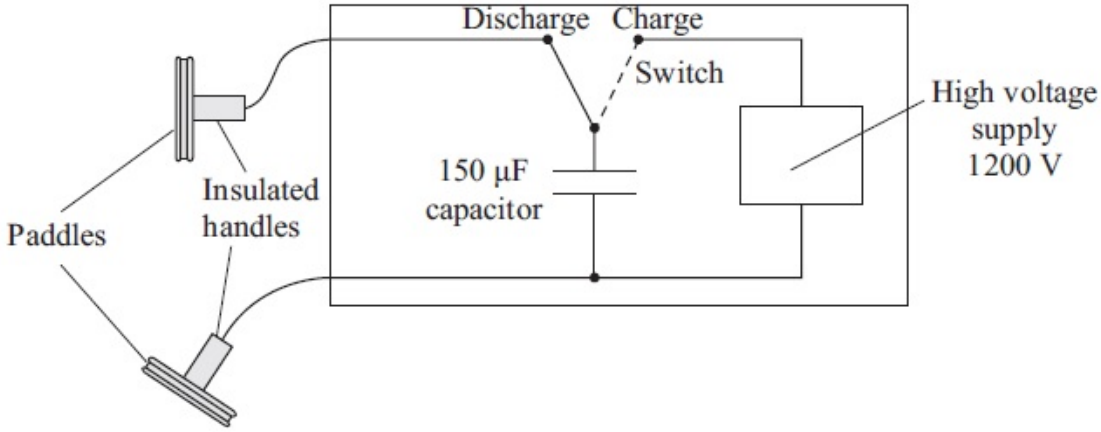The machine includes a high voltage supply which is used to charge a capacitor. Two defibrillation 'paddles' are placed on the chest of the patient and the capacitor is discharged through the patient.



(a) The 150 µF capacitor is first connected across the 1200 V supply

Calculate the charge on the capacitor.

(2)

.....

.....

Charge = ...

(b) Calculate the energy stored in the capacitor.

(2)

.....

.....

.....

Energy stored = ...

(c) When the capacitor discharges there is an initial current of 14 A in the chest of the patient.

(i) Show that the electrical resistance of the body tissue between the paddles is about 90 Ω

(1)

.....

.....

(ii) Calculate the time it will take for three quarters of the charge on the capacitor to discharge through the patient.

(3)

.....

.....

.....

.....

.....

Time = ...

(iii) Body resistance varies from person to person. If the body resistance was lower, the initial current would be greater.

State how this lower body resistance affects the charge passed through the body from the defibrillator.

(1)

.....

.....


.....

(Total for question = 9 marks)

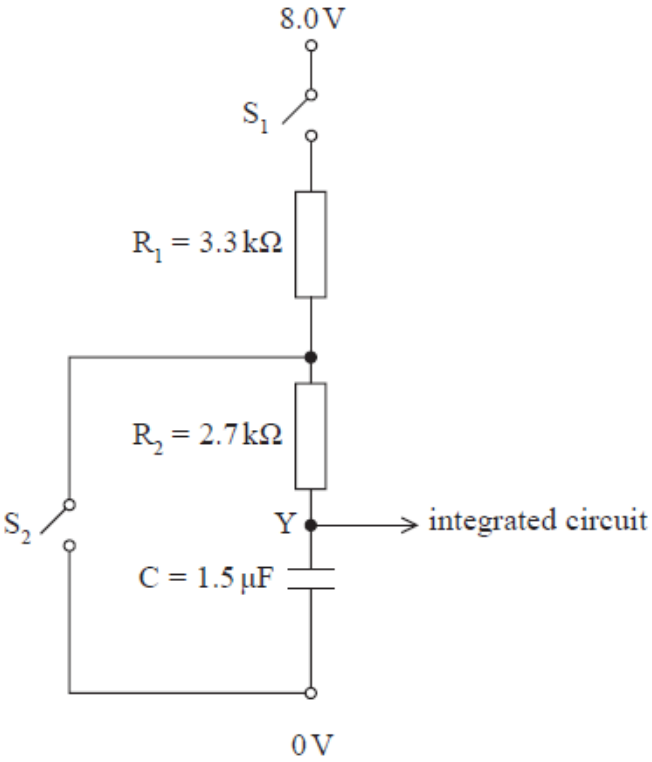Q5.

The properties of capacitors make them useful in timing circuits.

The following circuit is used to provide an input Y to an integrated circuit.



When the potential at Y is 8.0 V, the switch S_2 is closed.

(i) Calculate the time taken for the potential at Y to decrease to 2.0 V.

(3)

.....

.....

.....

.....

Time taken = ...

(ii) Calculate the energy stored on the capacitor when the potential at Y is 2.0 V.

(2)

.....

.....

.....

.....

Energy stored = ...

(Total for question = 5 marks)

Q6.

A capacitor of 50 μF is charged to a potential difference of 12 V.

The energy stored on the charged capacitor in joules is given by

☒ **A** $0.5 \times 50 \times 10^{-6} \times 12^2$

☒ **B** $\frac{0.5 \times 50 \times 10^{-6}}{12^2}$

☒ **C** $\frac{0.5 \times 12^2}{50 \times 10^{-6}}$

☒ **D** $0.5 \times (50 \times 10^{-6})^2 \times 12$


(Total for question = 1 mark)

Q7.

Answer the question with a cross in the box you think is correct ☒. If you change your mind about an answer, put a line through the box ☒ and then mark your new answer with a cross ☒.

A capacitor is connected to a power supply and charged to a potential difference V_0.

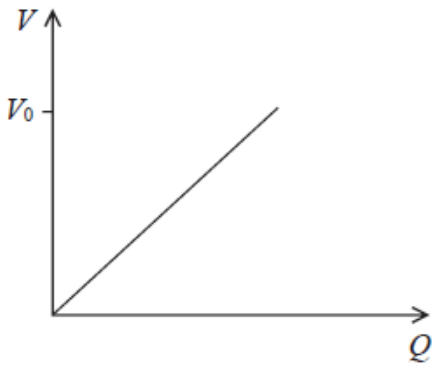The graph shows how the potential difference V across the capacitor varies with the charge Q on the capacitor.



At a potential difference V_0 a small charge ΔQ is added to the capacitor. This results in a small increase in potential difference ΔV across the capacitor.

Which of the following gives the approximate increase in energy stored on the capacitor due to this extra charge?

☒ **A** $\Delta V \times \Delta Q$

☒ **B** $\frac{\Delta V \times \Delta Q}{2}$

☒ **C** $V_0 \times \Delta Q$

☒ **D** $\frac{V_0 \times \Delta Q}{2}$

(Total for question = 1 mark)

Q8.

A capacitor of capacitance *C* has a potential difference *V* across it. The energy stored on the capacitor is Z joules. A second capacitor of capacitance *C*/2 has a potential difference 2*V* across it.
The energy stored on the second capacitor is

☒ **A** Z

☒ **B** 2Z

☒ **C** 4Z


☒ **D** 8Z

(Total for question = 1 mark)

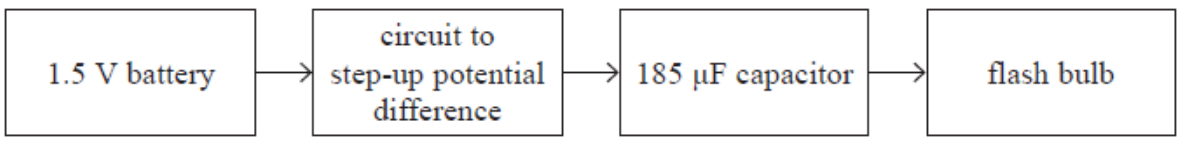Q9.

* Cameras usually have an inbuilt flash bulb that can be used to take photographs in poor light conditions. As a photograph is taken, the bulb should be able to produce a bright flash of light for up to 4 ms.

A capacitor can be used along with a battery as a power supply for the flash bulb. The flow diagram shows a possible arrangement.



Comment on the suitability of using this capacitor arrangement as a power supply rather than connecting the bulb directly to the battery.

A typical flash bulb has a resistance of 6 Ω.

(6)

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(Total for question = 6 marks)

Q10.

A capacitor of capacitance *C* is charged to a potential difference *V* by a power supply.
The energy stored on the charged capacitor is *W*.

What would be the energy stored if the potential difference were 2*V*?

(1)

☒ **A** $\frac{W}{4}$

☒ **B** $\frac{W}{2}$


☒ **C** $2W$

☒ **D** $4W$


(Total for question = 1 mark)

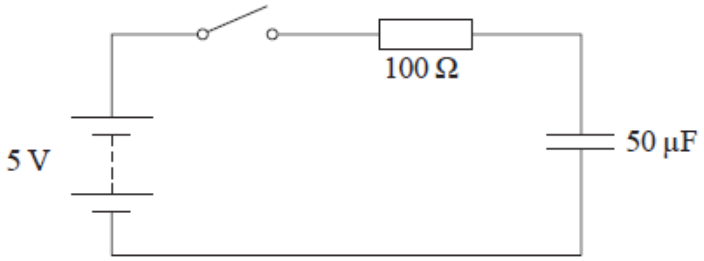Q1.


A circuit consists of a battery of e.m.f. 5 V and negligible internal resistance, a switch, a 100 Ω resistor and an uncharged 50 μF capacitor.



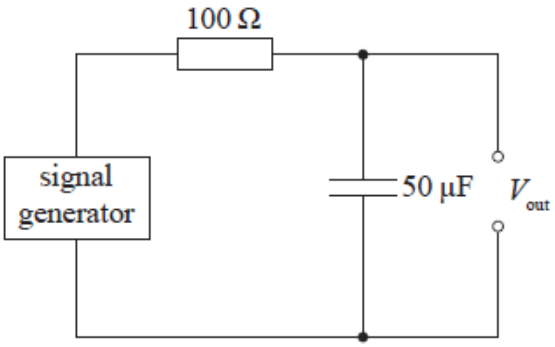The battery and switch are replaced by a signal generator providing a square wave output of peak potential difference 5 V. The signal generator has negligible internal resistance.



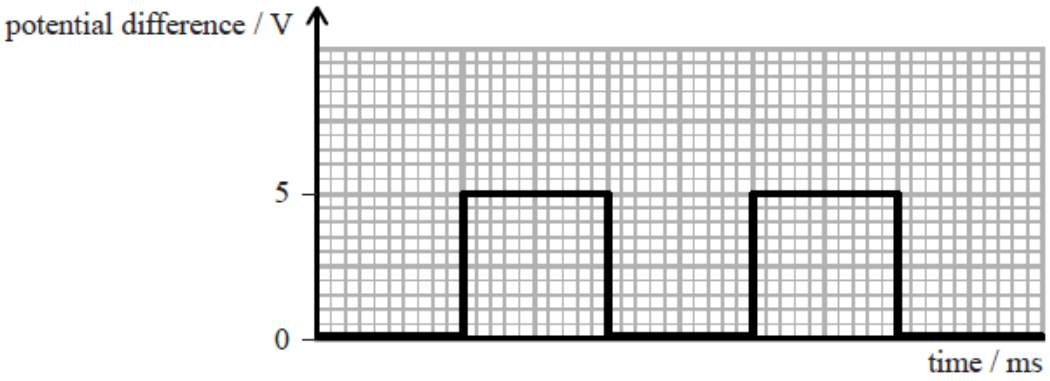The graph shows the square wave output of the signal generator. The frequency of the square wave is 20 Hz.



On the graph add values to the time axis and sketch a graph of the potential difference, V_{out}, across the capacitor for two cycles of the square wave. Assume the capacitor is initially uncharged.

(5)

.....

.....

.....


.....

.....

(Total for question = 5 marks)

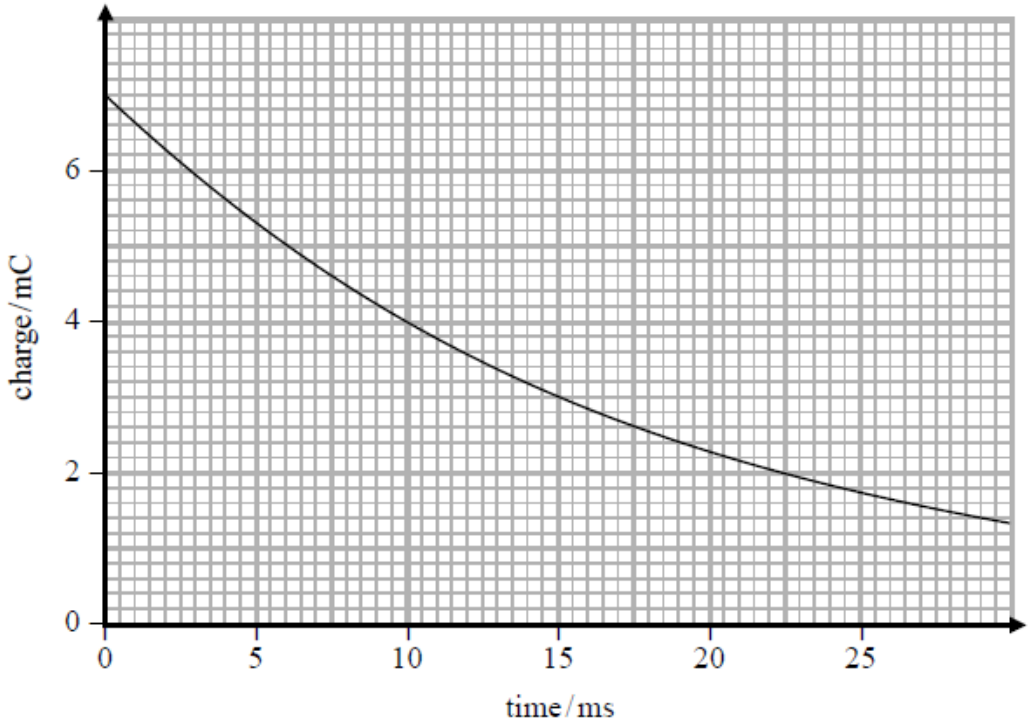Q2.

A capacitor is discharged through a resistor of resistance 900 Ω. The graph shows how the charge on the capacitor decreases with time.



Calculate the capacitance of the capacitor.

(4)

.....

.....

.....

.....

.....


.....

Capacitance = ...


(Total for question = 4 marks)

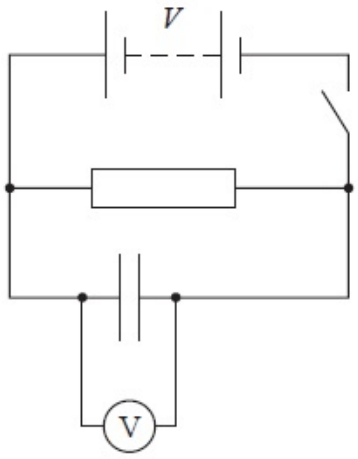Q3. The capacitor shown in the circuit below is initially charged to a potential difference (p.d.) *V* by closing the switch.

The power supply has negligible internal resistance.



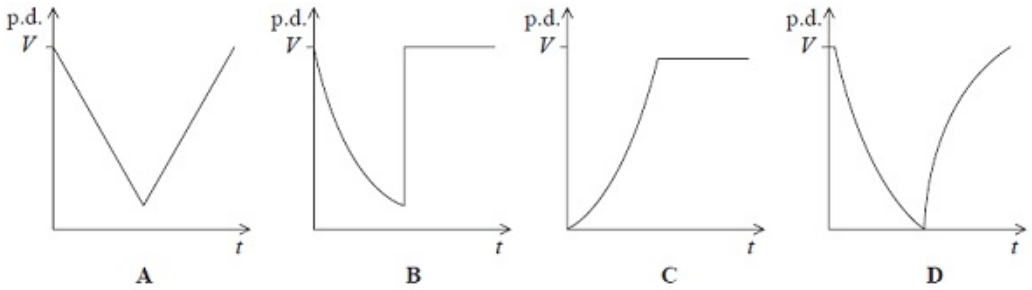The switch is opened and the p.d. across the capacitor allowed to fall. A short time later the switch is closed again. Select the graph that shows how the p.d. across the capacitor varies with time, after the switch is opened.



☒ **A**

☒ **B**

☒ **C**

☒ **D**

(Total for Question = 1 mark)

Q4. A student is investigating how the potential difference across a capacitor varies with time as the capacitor is charging.

He uses a 100 μF capacitor, a 5.0 V d.c. supply, a resistor, a voltmeter and a switch.

(a) (i) Draw a diagram of the circuit he should use.

(2)

(ii) Suggest why a voltage sensor connected to a data logger might be a suitable instrument for measuring the potential difference across the capacitor in this investigation.

(1)

.....

.....

(b) Calculate the maximum charge stored on the capacitor.

(2)

.....


.....

.....

.....

Charge = ...

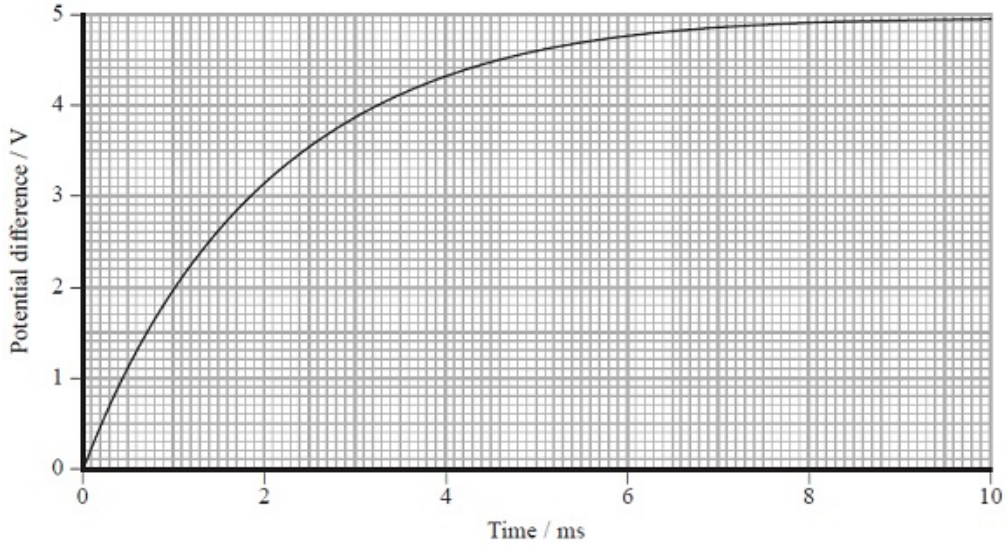(c) The graph shows how the potential difference across the capacitor varies with time as the capacitor is charging.



(i) Estimate the average charging current over the first 10 ms.

(2)

.....

.....

.....

Average charging current = ...

(ii) Use the graph to estimate the initial rate of increase of potential difference across the

capacitor and hence find the initial charging current.

(3)

.....

.....

.....

.....

.....

.....

.....

Initial charging current = ...

(iii) Use the value of the initial charging current to find the resistance of the resistor.

(2)

.....

.....

.....

.....

Resistance = ...

(Total for Question = 12 marks)

Q5. A particular experiment requires a very large current to be provided for a short time.

(a) An average current of 2.0×10^3 A is to be supplied to a coil of wire for a time of 1.4×10^{-3} s. The resistance of the coil is 0.50 Ω.

(i) Show that the charge that flows through the coil during this time is about 3 C.


(2)

.....

.....

.....

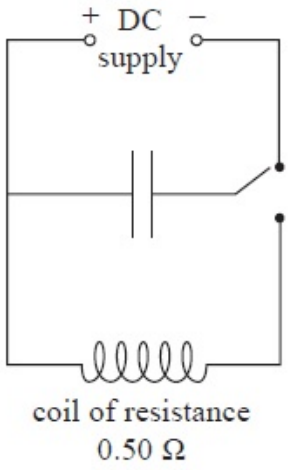(ii) The circuit shows how a capacitor could be charged and then discharged through the coil to provide the current.



The circuit contains a capacitor of capacitance 600 μF. This capacitor is suitable to provide the current for 1.4×10^{-3} s.

Explain why the capacitor is suitable.

(3)

.....

.....

.....

.....

.....

.....

(b) It can be assumed that the 600 μF capacitor completely discharges in 1.4×10^{-3} s.

(i) Calculate the potential difference of the power supply.

(2)

.....

.....

.....

Potential difference = ...

(ii) Calculate the average power delivered to the coil in this time.

(3)

.....

.....

.....

.....

.....

.....

Average power = ...

(Total for Question = 10 marks)

Q6.

In recent years there has been a development of ultracapacitors which have much higher capacitance than traditional capacitors. Capacitors store energy due to charge in an electric field whereas batteries store energy due to a chemical reaction. There are several applications where ultracapacitors have an advantage over batteries; for example storing energy from rapidly fluctuating supplies or delivering charge very quickly.

(a) A typical ultracapacitor has a capacitance of 1500 F and a maximum operating potential difference of 2.6 V.

(i) Show that the charge on this capacitor when fully charged is about 4000 C.

(2)


.....

.....

.....

(ii) Complete the graph on the axes below to show how the potential difference varies with charge for this capacitor.

(2)

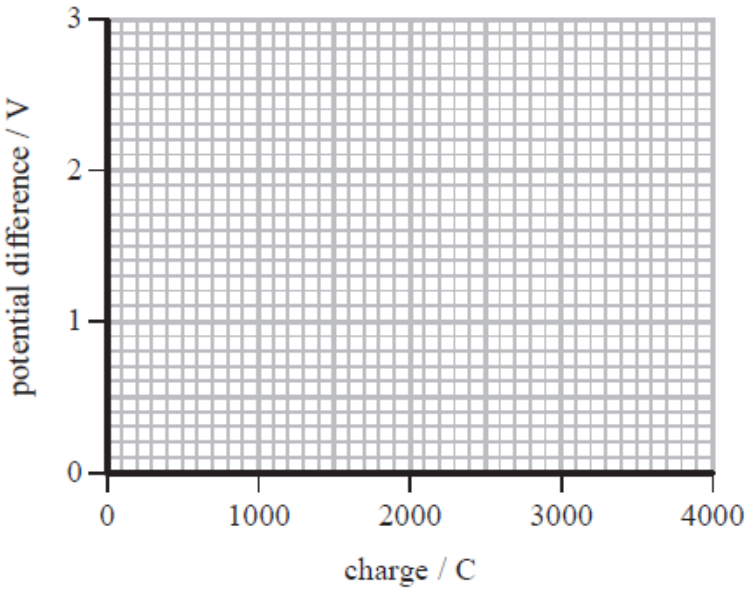

(iii) Calculate the energy stored in this capacitor when fully charged.

(2)


.....

.....

.....

Energy = ...

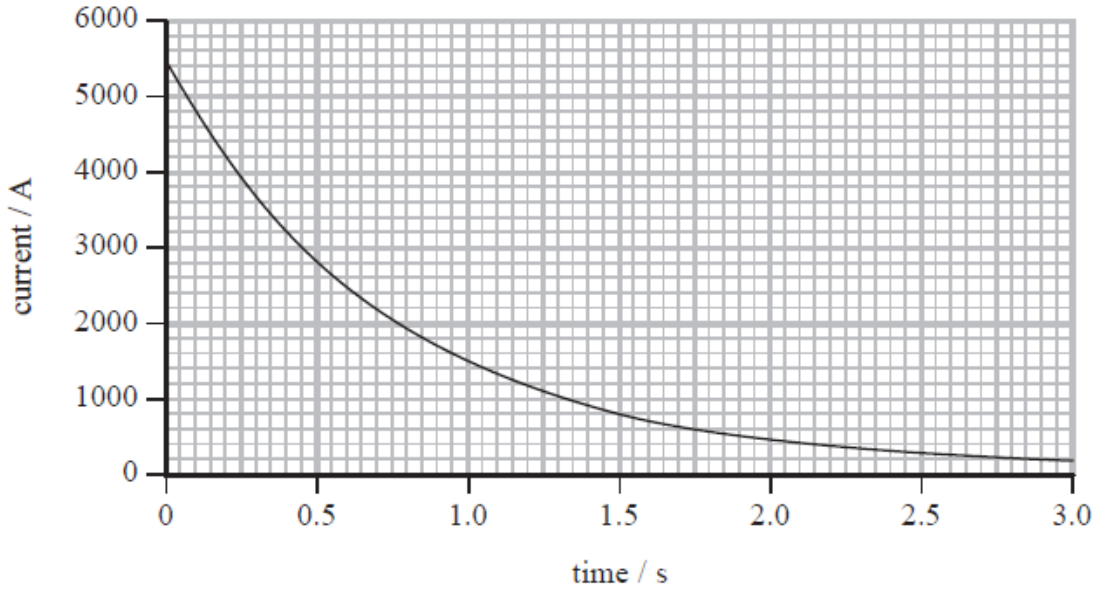(b) The graph below shows how the current varies with time as the capacitor is discharged through a circuit.



(i) Describe and explain the shape of the graph.

(2)

.....

.....

.....

.....

.....

(ii) Calculate the resistance of the circuit.

(4)

.....

.....

.....

.....

.....

Resistance = ...

(c) There is a limit to the amount of charge an ultracapacitor can hold but it can deliver the charge very quickly. A battery can deliver much more charge but only at a slower rate. For electric powered vehicles it is suggested that using a combination of batteries and ultracapacitors would give the best performance.

Suggest, with reasons, which stages of a journey would be more suited to ultracapacitors and which would be more suited to batteries.

(3)

.....

.....

.....

.....


.....

.....

(Total for question = 15 marks)

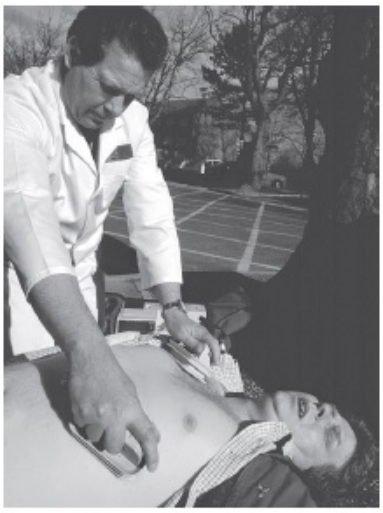
Q7.

A defibrillator is a machine that is used to correct an irregular heartbeat or to start the heart of someone who is in cardiac arrest.



The defibrillator passes a large current through the heart for a short time.

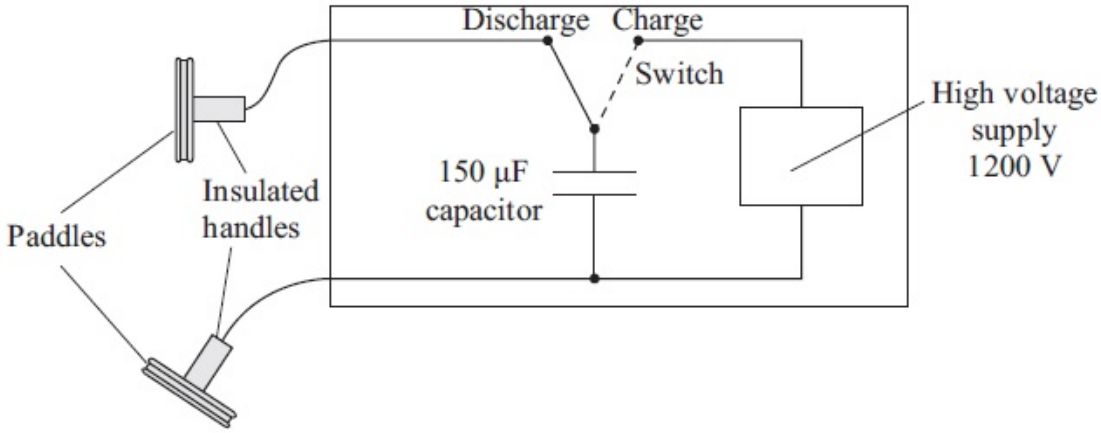The machine includes a high voltage supply which is used to charge a capacitor. Two defibrillation 'paddles' are placed on the chest of the patient and the capacitor is discharged through the patient.



(a) The 150 μF capacitor is first connected across the 1200 V supply

Calculate the charge on the capacitor.

(2)

.....

.....

Charge = ...

(b) Calculate the energy stored in the capacitor.

(2)

.....

.....

.....

Energy stored = ...

(c) When the capacitor discharges there is an initial current of 14 A in the chest of the patient.

(i) Show that the electrical resistance of the body tissue between the paddles is about 90 Ω

(1)

.....

.....

(ii) Calculate the time it will take for three quarters of the charge on the capacitor to discharge through the patient.

(3)

.....

.....

.....

.....

.....

Time = ...

(iii) Body resistance varies from person to person. If the body resistance was lower, the initial current would be greater.

State how this lower body resistance affects the charge passed through the body from the defibrillator.

(1)

.....

.....

.....

(Total for question = 9 marks)

Q8.

Some mobile phones have a capacitor touch screen made up of a sheet of glass with a thin metallic coating. The screen is charged and when it is touched some of the charge is transferred to the user. This causes a drop in electrical potential at the point where the screen is touched.

A capacitor is charged by connecting it across a battery and then discharged through a resistor. In the case of the touch screen the user provides a discharge resistance of about 900 Ω.

Explain how the capacitor discharges.

(3)

.....

.....

.....

.....

.....


.....

(Total for question = 3 marks)

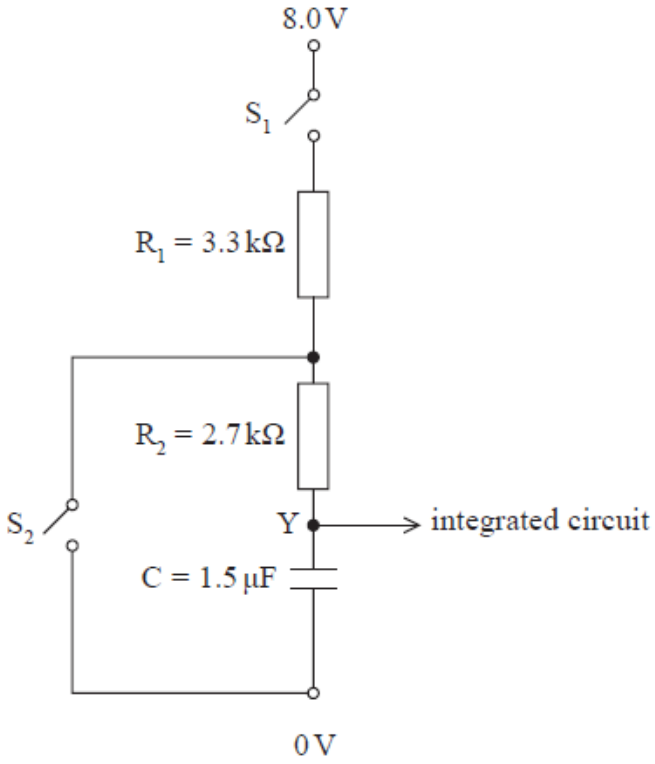Q9.

The properties of capacitors make them useful in timing circuits.

The following circuit is used to provide an input Y to an integrated circuit.




Initially the capacitor is uncharged. The switch S_1 is closed.

Sketch a graph to show how the potential at point Y varies with time.

(3)

.....

.....

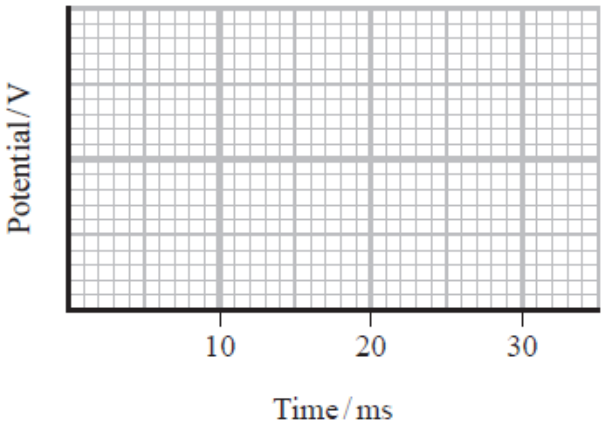


(Total for question = 3 marks)

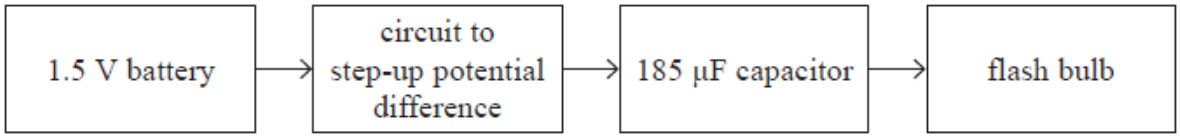Q10.

* Cameras usually have an inbuilt flash bulb that can be used to take photographs in poor light conditions. As a photograph is taken, the bulb should be able to produce a bright flash of light for up to 4 ms.

A capacitor can be used along with a battery as a power supply for the flash bulb. The flow diagram shows a possible arrangement.



Comment on the suitability of using this capacitor arrangement as a power supply rather than connecting the bulb directly to the battery.

A typical flash bulb has a resistance of 6 Ω.

(6)

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....


(Total for question = 6 marks)

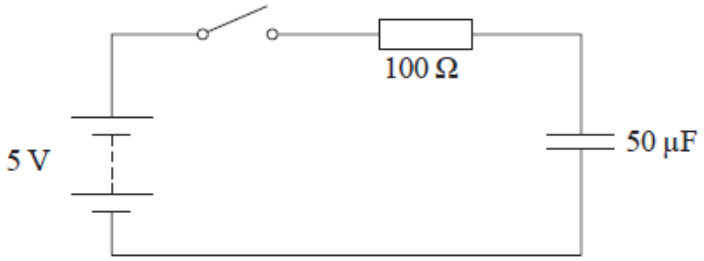Q1.


A circuit consists of a battery of e.m.f. 5 V and negligible internal resistance, a switch, a 100 Ω resistor and an uncharged 50 μF capacitor.



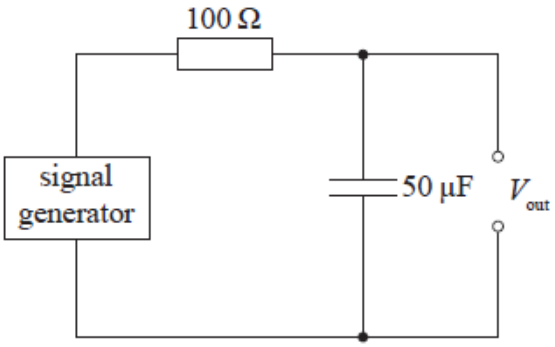The battery and switch are replaced by a signal generator providing a square wave output of peak potential difference 5 V. The signal generator has negligible internal resistance.



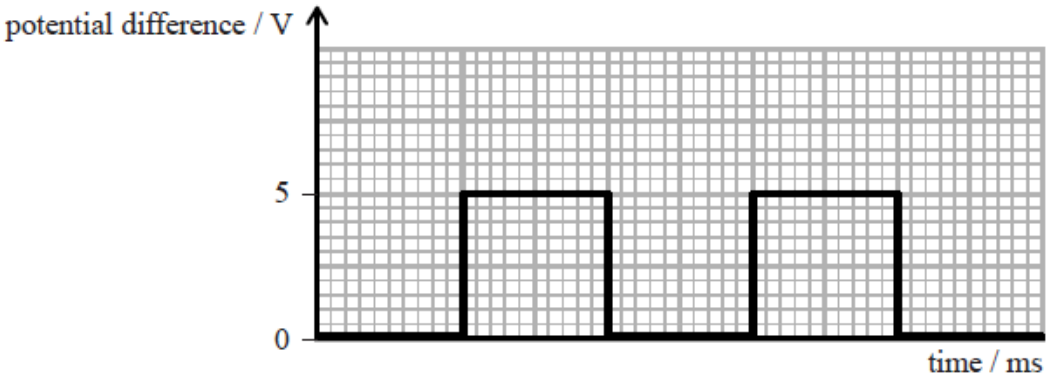The graph shows the square wave output of the signal generator. The frequency of the square wave is 20 Hz.



On the graph add values to the time axis and sketch a graph of the potential difference, V_{out}, across the capacitor for two cycles of the square wave. Assume the capacitor is initially uncharged.

(5)

.....

.....

.....


.....

.....

(Total for question = 5 marks)

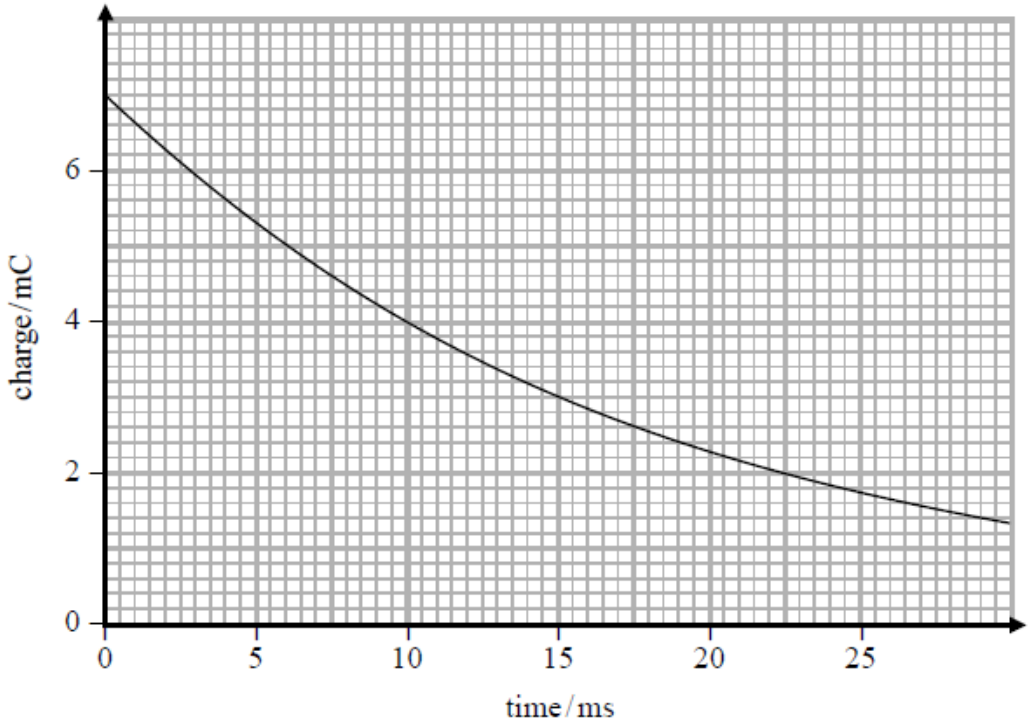Q2.

A capacitor is discharged through a resistor of resistance 900 Ω. The graph shows how the charge on the capacitor decreases with time.



Calculate the capacitance of the capacitor.

(4)

.....

.....

.....

.....

.....

.....

Capacitance = ...

(Total for question = 4 marks)

Q3.

A defibrillator is an electrical device designed to deliver a brief electrical signal to restore a normal rhythm to the heart. Electrodes are attached to the chest of a patient and a charged capacitor is discharged through the chest cavity.

In one defibrillator a 56 μF capacitor is charged by a potential difference of 2500 V.
During the discharge of the capacitor the resistance between the electrodes is 45 Ω.

Show that the time taken for 99% of the discharge to take place is about 12 ms and hence calculate the average current delivered by the defibrillator during this period.

(6)

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

Average current = ...

(Total for question = 6 marks)

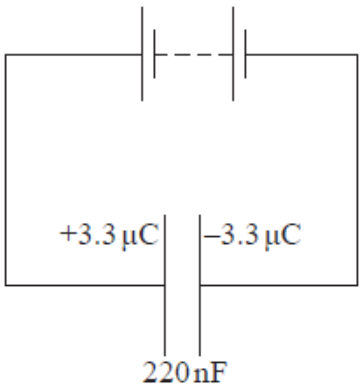Q4.

A capacitor is charged by a battery as shown in the circuit diagram.



(a) Calculate the e.m.f. of the battery and the energy stored in the charged capacitor.

(4)

.....

.....

.....

.....

.....

E.m.f. = ...

Energy = ...

(b) The capacitor is disconnected from the battery and discharged through a 20 MΩ resistor.

Calculate the time taken for 80% of the charge on the capacitor to discharge through the resistor.

(3)

.....

.....

.....

.....

.....

.....

.....

Time taken = ...

(c) Use an equation to explain whether the time taken for the capacitor to lose half its energy is greater or less than the time taken to lose half its charge.

(3)

.....

.....

.....

.....

.....

.....

(d) A student carries out an experiment to record data so that she can plot a graph of potential difference against time as the capacitor discharges.

State **two** advantages of using a datalogger rather than a voltmeter and stopwatch to record this data.

(2)

.....

.....

.....

.....

(Total for question = 12 marks)

Q5.

In recent years there has been a development of ultracapacitors which have much higher capacitance than traditional capacitors. Capacitors store energy due to charge in an electric field whereas batteries store energy due to a chemical reaction. There are several applications where ultracapacitors have an advantage over batteries; for example storing energy from rapidly fluctuating supplies or delivering charge very quickly.

(a) A typical ultracapacitor has a capacitance of 1500 F and a maximum operating potential difference of 2.6 V.

(i) Show that the charge on this capacitor when fully charged is about 4000 C.

(2)


.....

.....

.....

(ii) Complete the graph on the axes below to show how the potential difference varies with charge for this capacitor.

(2)

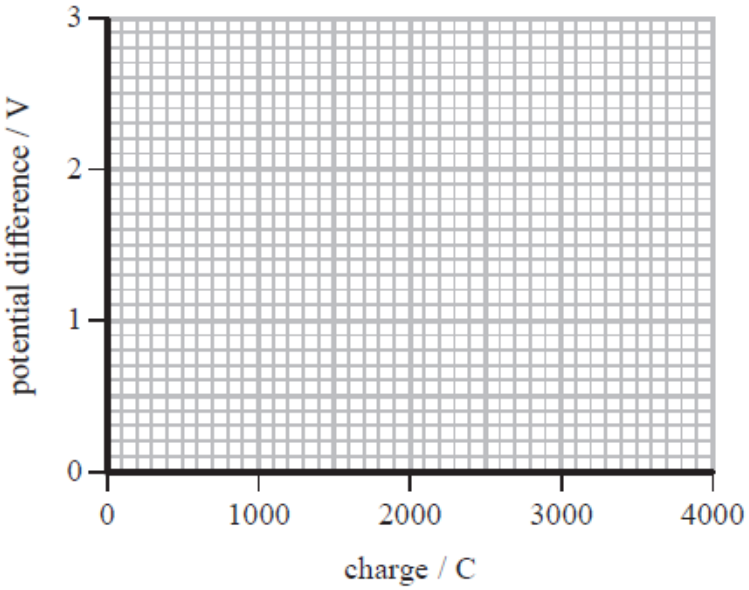

(iii) Calculate the energy stored in this capacitor when fully charged.

(2)


.....

.....

.....

Energy = ...

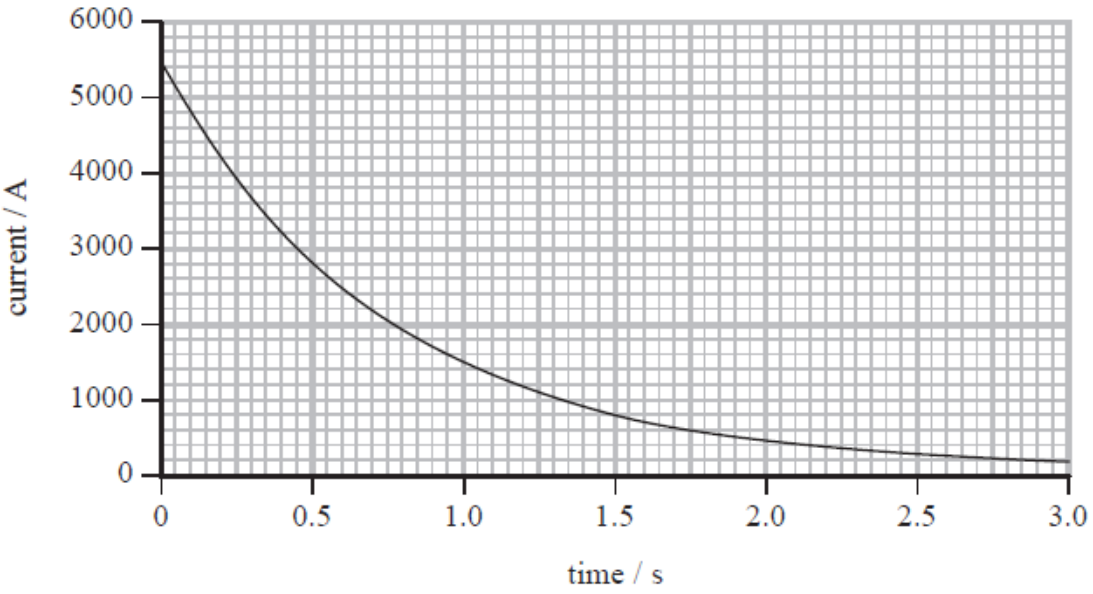(b) The graph below shows how the current varies with time as the capacitor is discharged through a circuit.



(i) Describe and explain the shape of the graph.

(2)

.....

.....

.....

.....

.....

(ii) Calculate the resistance of the circuit.

(4)

.....

.....

.....

.....

.....

Resistance = ...

(c) There is a limit to the amount of charge an ultracapacitor can hold but it can deliver the charge very quickly. A battery can deliver much more charge but only at a slower rate. For electric powered vehicles it is suggested that using a combination of batteries and ultracapacitors would give the best performance.

Suggest, with reasons, which stages of a journey would be more suited to ultracapacitors and which would be more suited to batteries.

(3)

.....

.....

.....

.....

.....

.....


(Total for question = 15 marks)

Q6.


Power supplies provide either alternating or direct currents and potential differences.

It is possible to convert alternating currents and p.d.s, to direct currents and p.d.s using diodes.

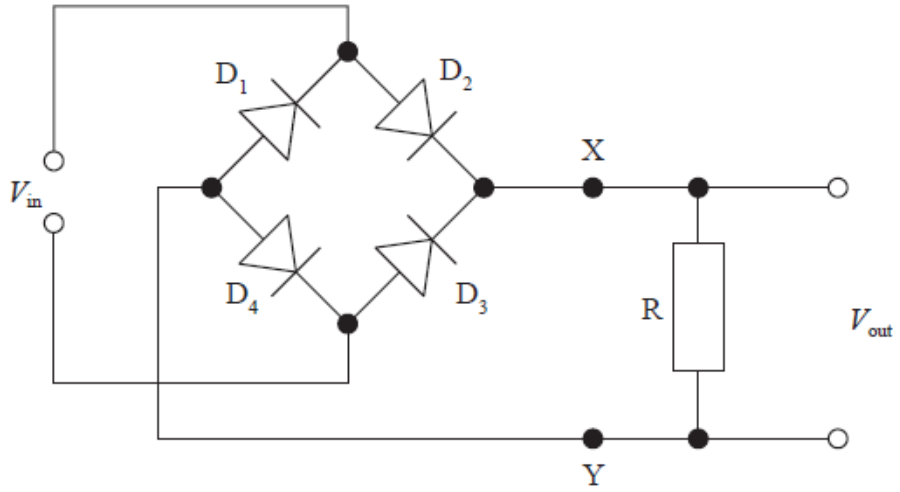The power supply provides an input V_{in} to the circuit shown. The circuit includes four diodes D_1, D_2, D_3 and D_4 and a resistor R. The circuit produces an output potential difference V_{out} .



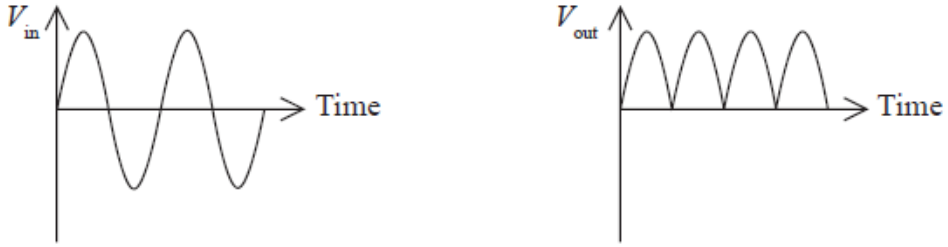A graph of V_{in} against time and a corresponding graph of V_{out} against time are shown below.



(i) Explain the operation of this circuit. Your answer should refer to D_1, D_2, D_3 and D_4.

(3)

.....

.....

.....


.....

.....

.....

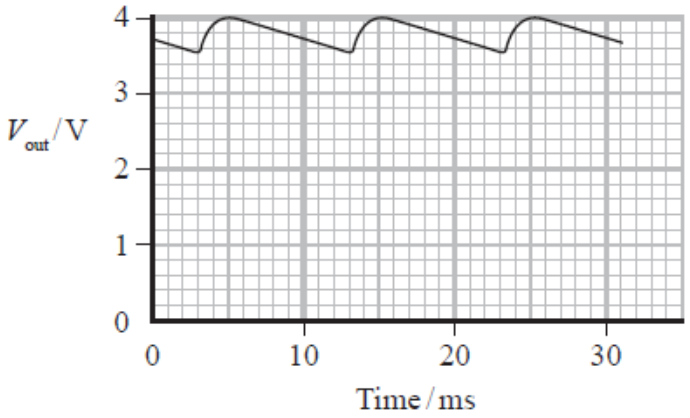(ii) A capacitor is added between points X and Y in the circuit.

The new graph of V_{out} against time is shown below.



Determine a value for the capacitance of the capacitor.

resistance of R = 2.2 kΩ

(3)

.....

.....

.....

.....

.....

.....


.....

Capacitance = ...

(Total for question = 6 marks)

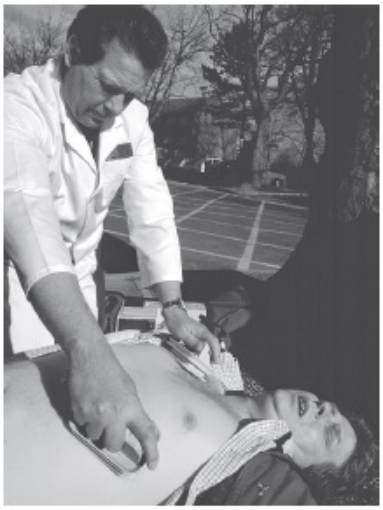
Q7.

A defibrillator is a machine that is used to correct an irregular heartbeat or to start the heart of someone who is in cardiac arrest.



The defibrillator passes a large current through the heart for a short time.

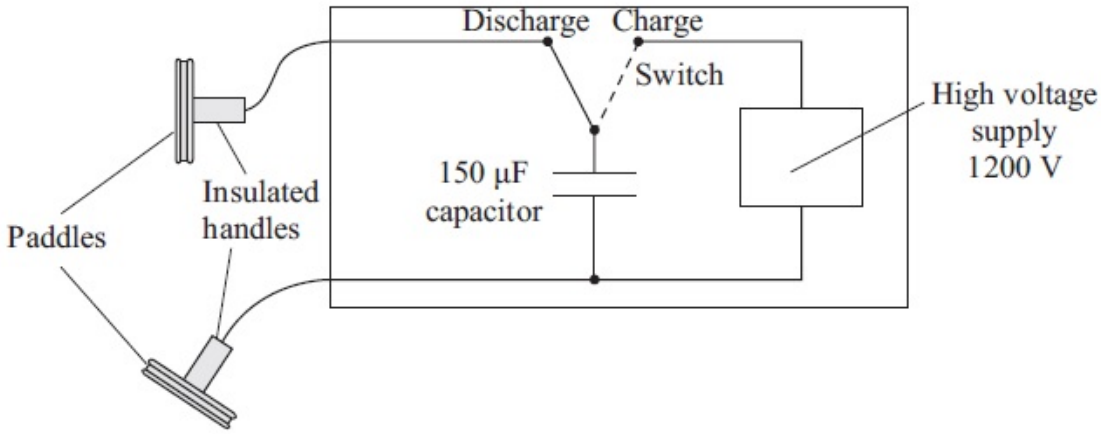The machine includes a high voltage supply which is used to charge a capacitor. Two defibrillation 'paddles' are placed on the chest of the patient and the capacitor is discharged through the patient.



(a) The 150 µF capacitor is first connected across the 1200 V supply

Calculate the charge on the capacitor.

(2)

.....

.....

Charge = ...

(b) Calculate the energy stored in the capacitor.

(2)

.....

.....

.....

Energy stored = ...

(c) When the capacitor discharges there is an initial current of 14 A in the chest of the patient.

(i) Show that the electrical resistance of the body tissue between the paddles is about 90 Ω

(1)

.....

.....

(ii) Calculate the time it will take for three quarters of the charge on the capacitor to discharge through the patient.

(3)

.....

.....

.....

.....

.....

Time = ...

(iii) Body resistance varies from person to person. If the body resistance was lower, the initial current would be greater.

State how this lower body resistance affects the charge passed through the body from the defibrillator.

(1)

.....

.....

.....

(Total for question = 9 marks)

Q8.

Some mobile phones have a capacitor touch screen made up of a sheet of glass with a thin metallic coating. The screen is charged and when it is touched some of the charge is transferred

to the user. This causes a drop in electrical potential at the point where the screen is touched.

A capacitor is charged by connecting it across a battery and then discharged through a resistor. In the case of the touch screen the user provides a discharge resistance of about 900 Ω.

Explain how the capacitor discharges.

(3)

.....

.....

.....

.....

.....


.....

(Total for question = 3 marks)

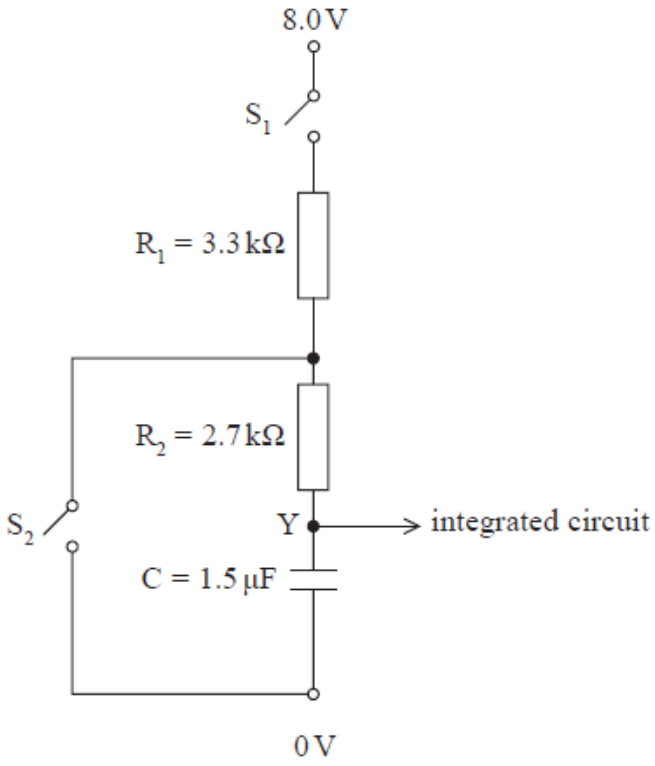Q9.

The properties of capacitors make them useful in timing circuits.

The following circuit is used to provide an input Y to an integrated circuit.



When the potential at Y is 8.0 V, the switch S_2 is closed.

(i) Calculate the time taken for the potential at Y to decrease to 2.0 V.

(3)

.....

.....

.....

.....

Time taken = ...

(ii) Calculate the energy stored on the capacitor when the potential at Y is 2.0 V.

(2)

.....

.....

.....

.....

Energy stored = ...

(Total for question = 5 marks)

Q10.

A simple model of the hydrogen atom consists of an electron moving in a circular path around a proton.

(i) In this simple model it is the electrostatic force, rather than the gravitational force, that is responsible for keeping the electron in a circular path.

By means of calculations justify this statement.

radius r of the hydrogen atom = 5.3×10^{-11} m

(4)

.....

.....

.....

.....

.....

(ii) Ignoring the gravitational force, calculate the velocity of the electron in this simple model of the hydrogen atom.

(3)

.....

.....

.....

.....

.....

Velocity = ...

(Total for question = 7 marks)